



7474 Decade Counter

sunkari kalpana
Roll No: FWC22307
kalpanamudhiraj@gmail.com

I. ABSTRACT

This paper shows how to use the 7474 D-Flip Flop ICs in a sequential circuit to realize a decade counter using arduino uno.

II. COMPONENTS

The required components list is given in Table: I., seven segment display is shown in Fig.1, IC 7447 diagram is shown in Fig.2 and 7474 D-Flip Flop pin diagram is shown in Fig-3.

Components	Value	Quantity
IC	7447	1
IC	7474	2
seven segment display		1
Arduino	UNO	1
Jumper Wires		50
Breadboard		1

TABLE I

IV. RESULTS

- 1) Download the code given in the link below and execute them to see the output as shown in Fig.6.
- 2) <https://github.com/rajib05ra/FWC-Assignments/tree/main/Assignment>

V. CONCLUSION

Hence implementation of 7474 IC Decade Counter on Seven segment display using arduino UNO is done.

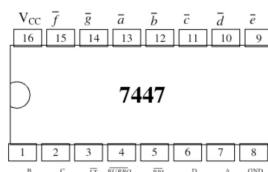


Fig. 1.

III. PROCEDURE

- 1) Make the connections of arduino, 7447 and two 7474 ICs according to Fig-4.
- 2) Block diagram of Decade Counter.
- 3) Execute the arduino code without any errors.
- 4) After upload the code into hardware setup using arduino IDE platform with hex file.

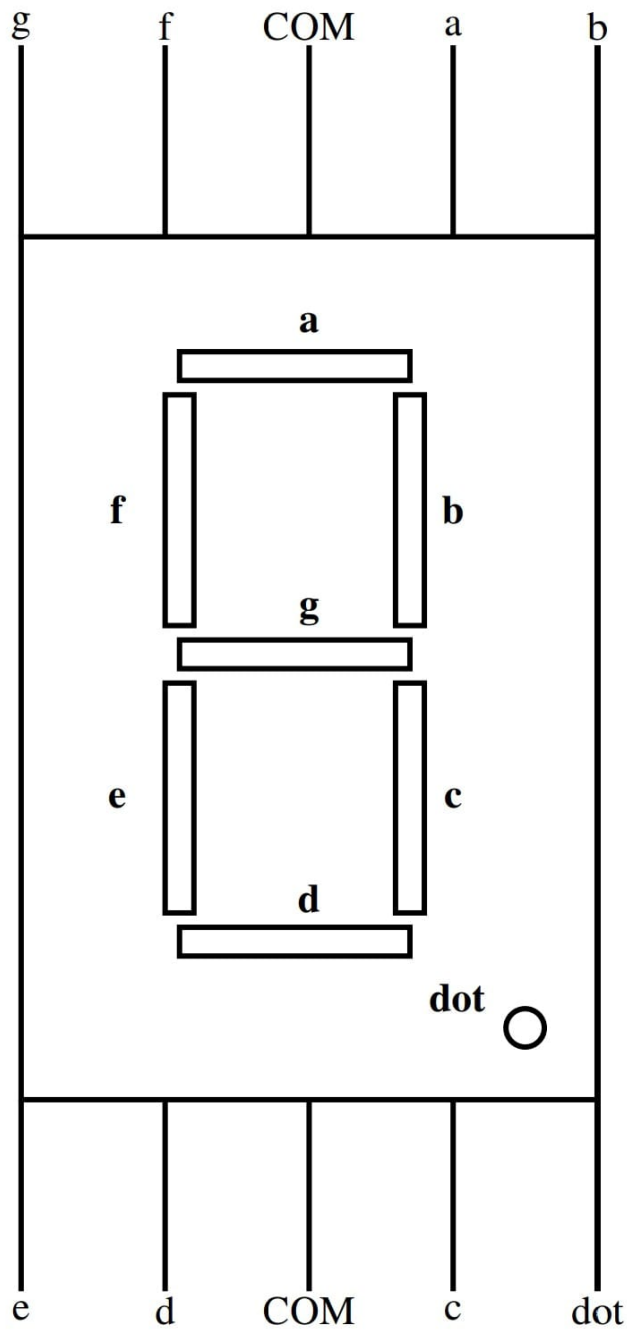


Fig. 2.

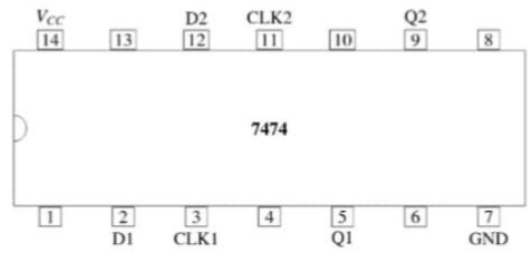


Fig. 3.

	INPUT				OUTPUT				CLOCK		5V			
	D6	D7	D8	D9	D2	D3	D4	D5	CLK1	CLK2	1	4	10	13
7474	5	9			2	12			CLK1	CLK2	1	4	10	13
7474			5	9		2	12		CLK1	CLK2	1	4	10	13
7447					7	1	2	6						

Fig. 4.

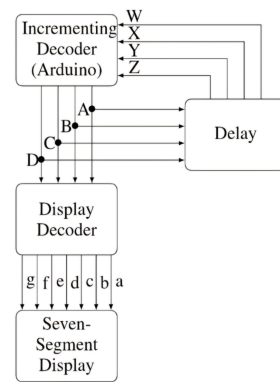


Fig. 5.

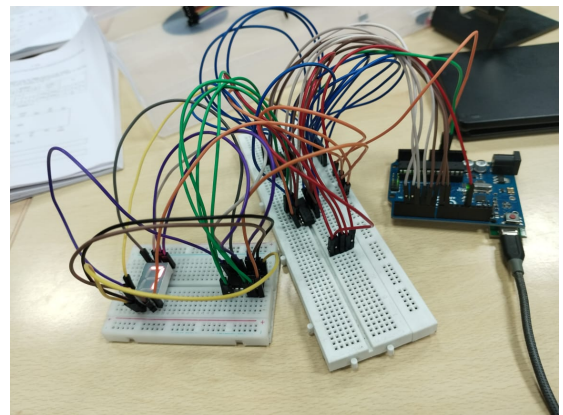


Fig. 6.