



K - Map Assignment

sunkari kalpana
Roll No: FWC22307
kalpanamudhirajgmail.com

I. ABSTRACT

This paper explains a Karnaugh maps (K-map) by finding the logic functions for the incrementing decoder from 0 to 9 and don't care condition using arduino uno.

II. COMPONENTS

The required components list is given in Table: I., seven segment display is shown in Fig.1, and 7447 IC pin diagram is shown in Fig-2.

| Components | Value | Quantity |
|-----------------------|-------|----------|
| IC | 7447 | 1 |
| seven segment display | | 1 |
| Arduino | UNO | 1 |
| Jumper Wires | | 50 |
| Breadboard | | 1 |

TABLE I

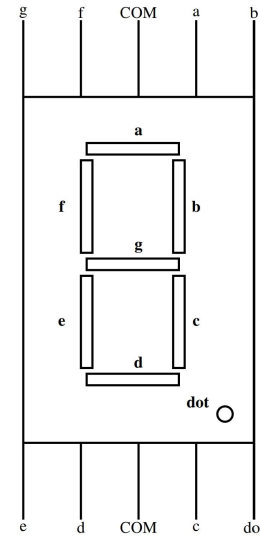


Fig. 1.



Fig. 2.

III. PROCEDURE

- 1) Make the connections of arduino, and 7447 ICs according to Fig-4.
- 2) Make the connections of seven segment display and 7447 IC as below fig-5.
- 3) Truth Table for k-map without don't care and incrementing from 0 to 9 :

| Z | Y | X | W | D | C | B | A |
|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |

TABLE II

- 4) Truth Table for k-map with don't care condition :
- 5) Execute the arduino code without any errors.
- 6) After upload the code into hardware setup using arduino IDE platform with hex file.

| 7447 | \bar{a} | \bar{b} | \bar{c} | \bar{d} | \bar{e} | \bar{f} | \bar{g} |
|---------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|
| Display | a | b | c | d | e | f | g |

Fig. 3.

| 7447 | D | C | B | A |
|---------|---|---|---|---|
| Arduino | 5 | 4 | 3 | 2 |

Fig. 4.

IV. RESULTS

- 1) Download the code given in the link below and execute them to see the output as shown in Fig.6,7.
- 2) <https://github.com/rajib05ra/FWC-Assignments/tree/main/Assignment>

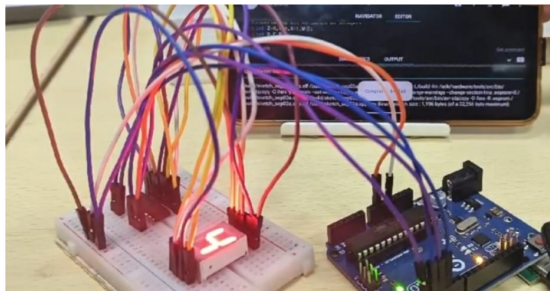


Fig. 5.

V. CONCLUSION

Hence implementation of K-Map using 7447 IC and Seven segment display using arduino UNO is done.

| Z | Y | X | W | D | C | B | A |
|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | - | - | - | - |
| 1 | 0 | 1 | 1 | - | - | - | - |
| 1 | 1 | 0 | 0 | - | - | - | - |
| 1 | 1 | 0 | 1 | - | - | - | - |
| 1 | 1 | 1 | 0 | - | - | - | - |
| 1 | 1 | 1 | 1 | - | - | - | - |

TABLE III